

Arduino 37 Sensor Kit

First acquaintance

Lecturer Dr. Samuel Kosolapov

General Appearance: ~ 36+1 modules in one box



In this presentation only simple (even primitive) modules will be explained and demonstrated

Leaflet inside the box



Leaflet inside the box: Arrangement of modules



List of Modules in the box: KY-0XY

- 1 x Small passive buzzer module KY-006
- 1 x 2-color LED module KY-011
- 1 x Hit sensor module KY-031
- 1 x Vibration switch module KY-002
- 1 x Photo resistor module KY-018
- 1 x Key switch module KY-004
- 1 x Tilt switch module KY-020
- 1 x 3-color full-color LED SMD modules KY-009
- 1 x Infrared emission sensor module KY-005
- 1 x 3-color LED module KY-016
- 1 x Mercury open optical module KY-017
- 1 x Yin Yi 2-color LED module 3MM KY-029
- 1 x Active buzzer module KY-012
- 1 x Temperature sensor module KY-013
- 1 x Automatic flashing colorful LED module KY-034
- 1 x Mini magnetic reed modules KY-021
- 1 x Hall magnetic sensor module KY-003
- 1 x Infrared sensor receiver module KY-022


- 1 x Class Bihor magnetic sensor KY-035
- 1 x Magic light cup module KY-027
- 1 x Rotary encoder module KY-040
- 1 x Optical broken module KY-010
- 1 x Detect the heartbeat module KY-039
- 1 x Reed module KY-025
- 1 x Obstacle avoidance sensor module KY-032
- 1 x Hunt sensor module KY-033
- 1 x Microphone sound sensor module KY-038
- 1 x Laser sensor module KY-008
- 1 x 5V relay module KY-019
- 1 x Temperature sensor module KY-001
- 1 x Temperature sensor module KY-028
- 1 x Linear magnetic Hall sensors KY-024
- 1 x Flame sensor module KY-026
- 1 x Sensitive microphone sensor module KY-037
- 1 x Temperature and humidity sensor module KY-015
- 1 x XY-axis joystick module KY-023
- 1 x Metal touch sensor module KY-036

Problem: Random Arrangement inside the box:

Modules are not arranged as in this picture.
→ First “**exercise**” is to **arrange** modules
in accordance with this picture

THIS IS NOT A TRIVIAL JOB !!!

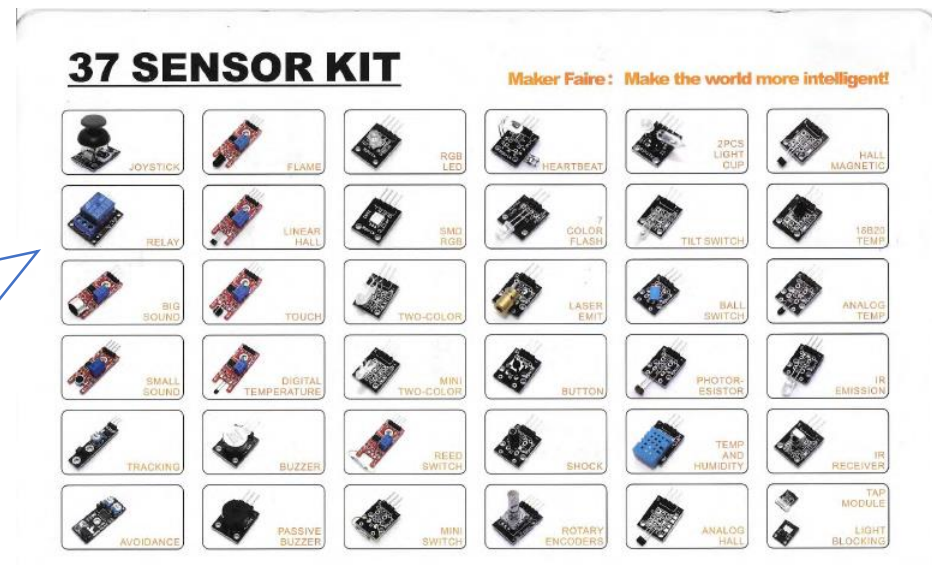Visual difference between some modules is very small.
(Remember “Find 2 differences games for children” ?
Small details (like “holes” position)
must be taken into account.





What is the difference ?

(KY number is not present on the board ...)


Arduino KY-006 Small
passive buzzer module

Arduino KY-012 **Active**
buzzer module

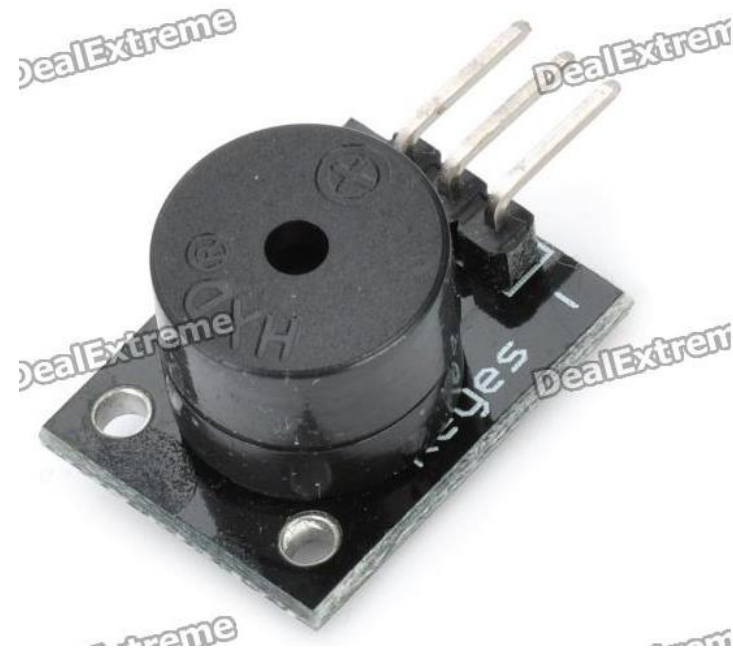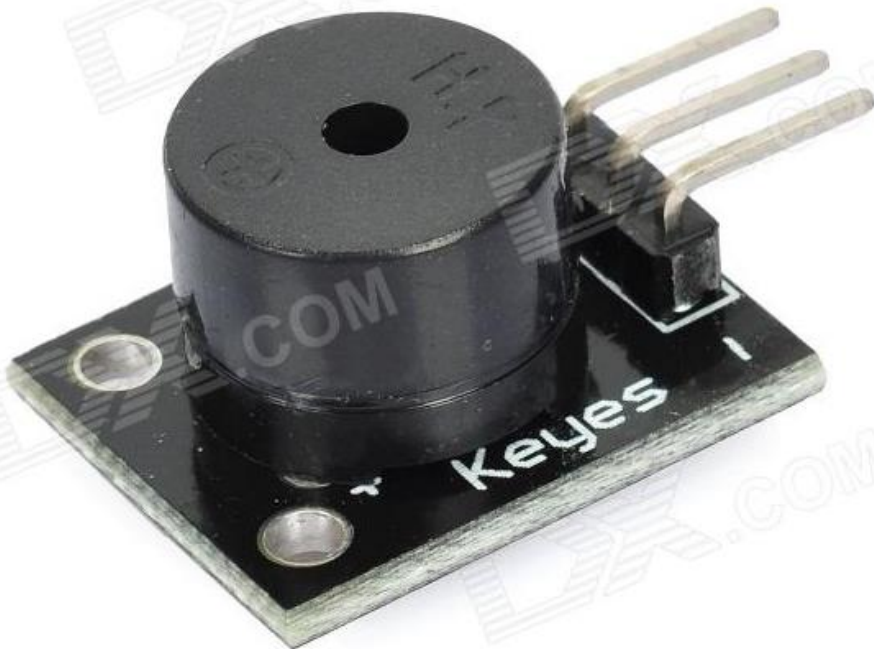

Simple “electronic” test (*demonstrate*)

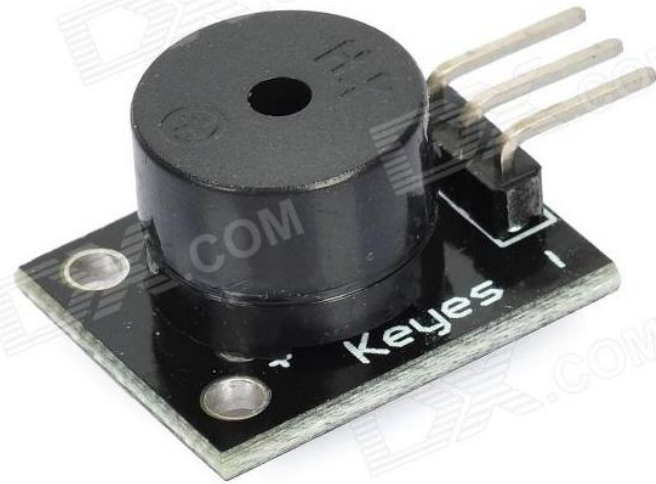passive buzzer module
will shortly “click”



Connect Pin “-” to GND
Connect Pin “S” to +5V
Middle Pin: is not important





Active buzzer module
will produce constant tone

**Execute “live test”
only after you get
proper explanations**

Details and usage later

Useful tool for EE: Magnification lens

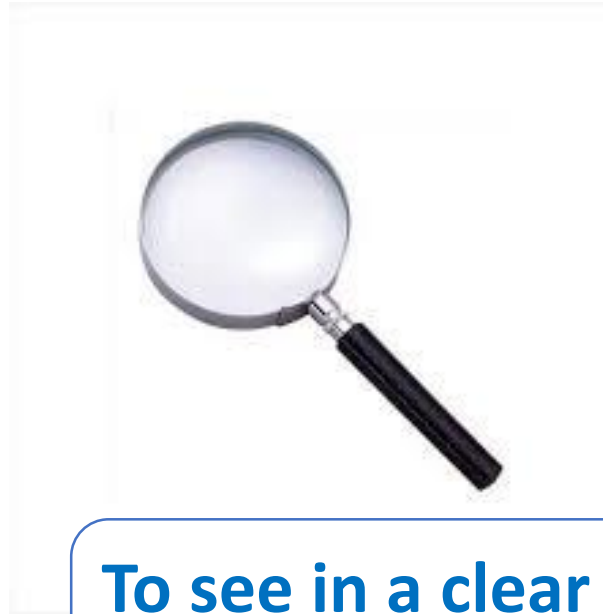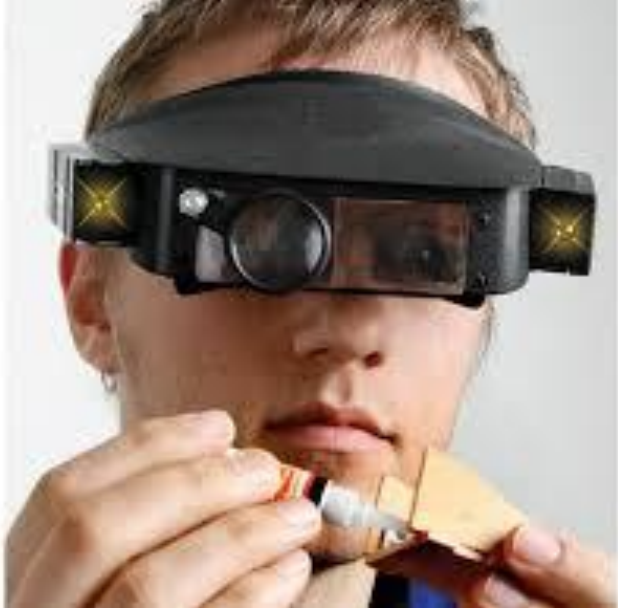

To see in a clear way
small letters and pin numbers

Some elements of the sensors
can be bend in an **inappropriate way**.

Gently unbend (or ask lecturer in case of doubts)

Problem: No serious documentation

The problem with finding the data sheet is due to the fact that the name on the controllers board KEYES is the name of the board manufacturer who does not specify his board anywhere

Their reference for the product is:
318-ENC130175F-12PS

The data sheet **is just one page** but it does describe the PIN_OUTS.

However, short module description + examples can be found:

https://tkkrlab.nl/wiki/Arduino_37_sensors

(Unfortunately, this site is Google Translation from Chinese, so some creativity is needed to understand what does this means...)

→ **One of the goals of student's presentations:**

Create some documents and examples

Hint: use "KY-xxx" to find youtube videos and exemplary projects

Primitive Sensor: Switch


37 Sensor Kit contains a number of primitive sensors which are actually operates as a mechanical switch. Despite primitive design , those modules **sense** important events.

In some cases operation of the “switch sensors” can be demonstrated by measuring resistance between “S” and GND pins


Pin “-” : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin “S” : Connect to Arduino Digital pin configured to INPUT

Between Pin “S” and Middle Pin (“+5V”) there is
10 k Pull-up resistor

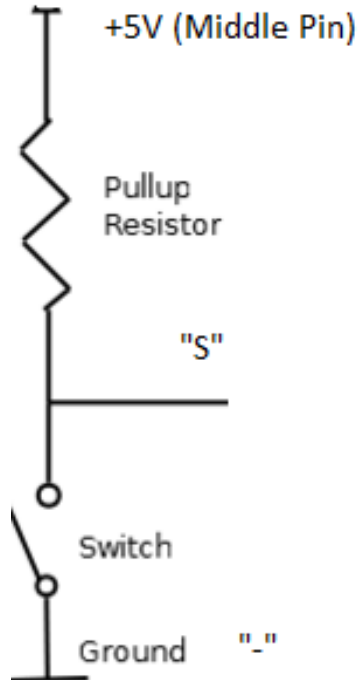Pull-Up resistor. Reminder:
It is assumed that input impedance
of the circuit connected to Pin “S” is high
and has no influence on the Pin “S” voltage.
When switch is OFF, pin “S” has “5V” (HIGH)
When switch is on, Pin “S” is connected to the Ground
→ Pin “S” is LOW



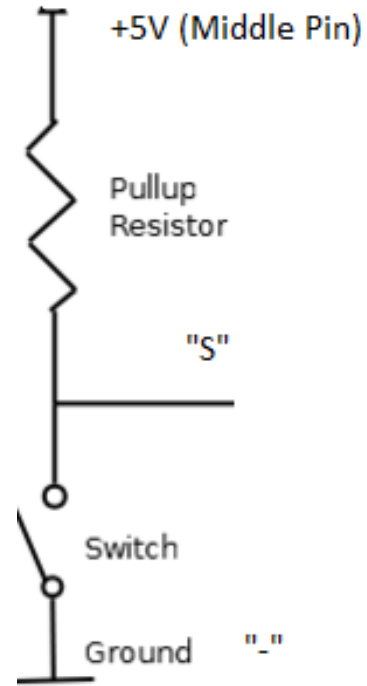Primitive Sensor: KY-004 Mechanical Key Switch




Pin "-" : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin "S" : Connect to Arduino Digital pin configured to INPUT

Between Pin "S" and Middle Pin ("+5V") there is
10 k Pull-up resistor

**Warning: Image is differ
from real switch (mirror)**

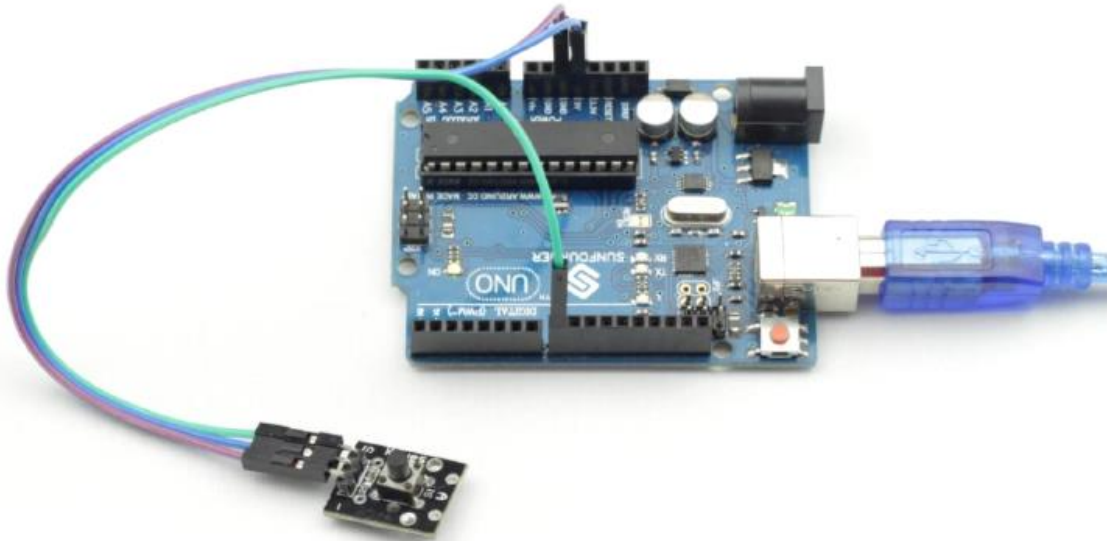Example of Mechanical Key Switch Test

Pin "S" of the switch connected to (say) Pin 8 of the Arduino Board



Circuit operation:
LED13 is normally OFF
When the button (key) is pressed, LED13 is ON



Example of Mechanical Key Switch Test

```
int Led = 13 ;// define LED Interface
int buttonpin = 10; // define the key switch sensor interface
int val ;// define numeric variables val
void setup ()
{
  pinMode (Led, OUTPUT); // define LED as output interface
  pinMode (buttonpin, INPUT); // define the key switch sensor output interface
}
void loop ()
{
  val = digitalRead (buttonpin);
  if (val == HIGH) // When the key switch when the sensor detects a signal, LED flashes
  {
    digitalWrite (Led, HIGH);
  }
  else
  {
    digitalWrite (Led, LOW);
  }
}
```

Pin 10 (and not 8) is used in this example

**No DEBOUNCING in this example !!!
(Human eye will “average” LED intensity changes)**

KY-021 Mini magnetic reed switch

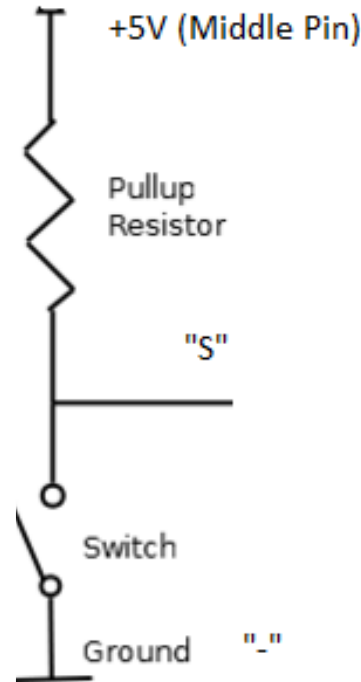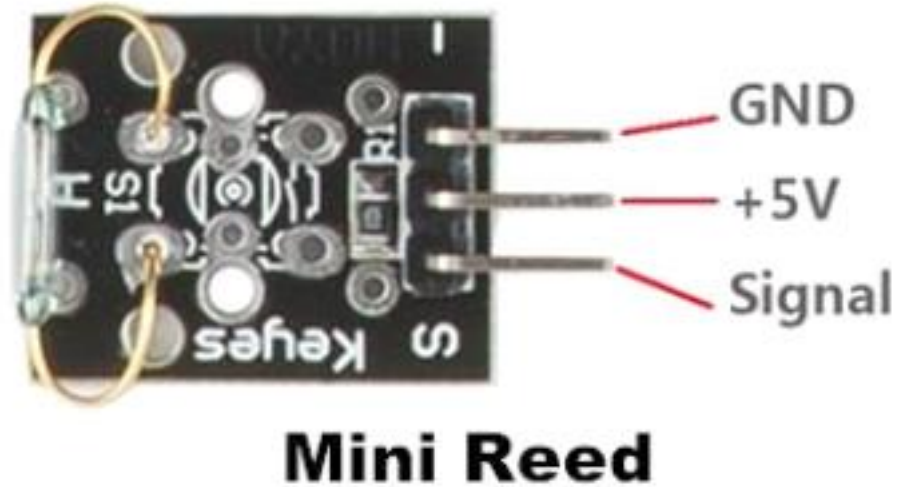

Pin "-" : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin "S" : Connect to Arduino Digital pin configured to INPUT


Between Pin "S" and Middle Pin ("+5V") there is 10 k Pull-up resistor

Switch is Normally OPEN.
When exposed to magnetic field switch get closed
(Demonstrate with tester and small magnet)

The code is as with "simple button/key switch
Discuss usage in the industry and at home.
(Hidden lock (open with magnet.
Door with magnet: is the door open ?

KY-021 Mini magnetic reed switch

Small magnet

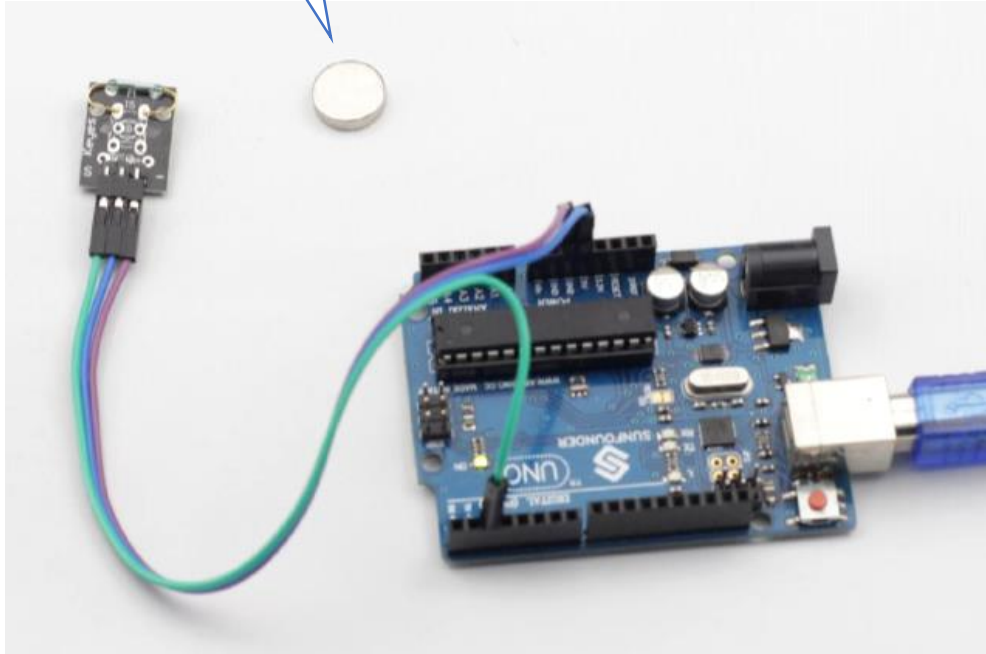

The shell of a reed switch is commonly a sealed glass pipe in which

two iron elastic reed electroplates are equipped and inert gases are filled.

Normally, the two reeds are separated.

However, when a magnetic substance (for example, small magnet) approaches the glass tube,

the two reeds in the glass tube are magnetized and attract each other

As a result, the two reeds will pull together creating electrical contact


After external magnetic force disappeared,

the two reeds will be separated with each other because they have the same magnetism, then the circuit is disconnected.

KY-020 Tilt switch



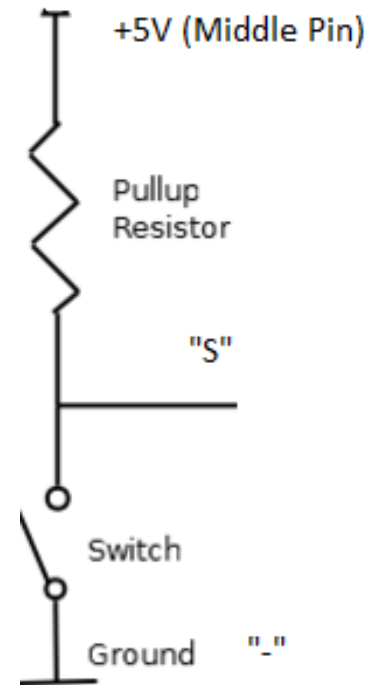Switch is Normally OPEN.
When oriented upwards, the switch is closed.
Inside: a small ball that moves when orientation changes
(Demonstrate with tester)




Pin "-" : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin "S" : Connect to Arduino Digital pin
configured to INPUT

Between Pin "S" and Middle Pin ("+5V")
there is 10 k Pull-up resistor


The code is as with "simple button/key switch

Discuss usage in the industry and at home.
(Theft protection ?
Alarm when object is moved ?

KY-002 Vibration switch

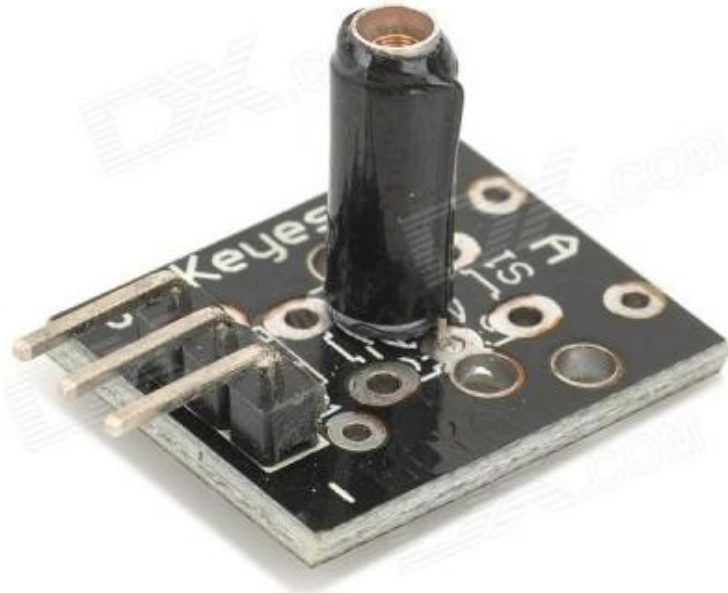

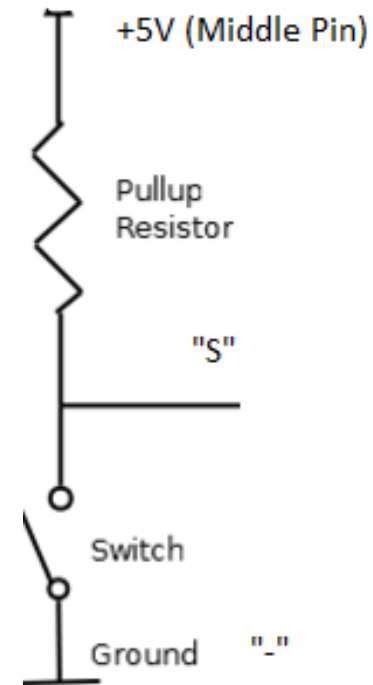A shock switch also called vibration switch, spring switch or shock sensor, is an electronic switch. It contains conductive vibration spring. Switch is normally open. When vibrated, switch is closed.





Pin “-” : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin “S” : Connect to Arduino Digital pin configured to INPUT

Between Pin “S” and Middle Pin (“+5V”) there is 10 k Pull-up resistor

The code is as with “simple button/key switch
Discuss usage in the industry and at home.

Operation of this module cannot be demonstrated by using multimeter (too slow)

KY-031 knock/tap switch

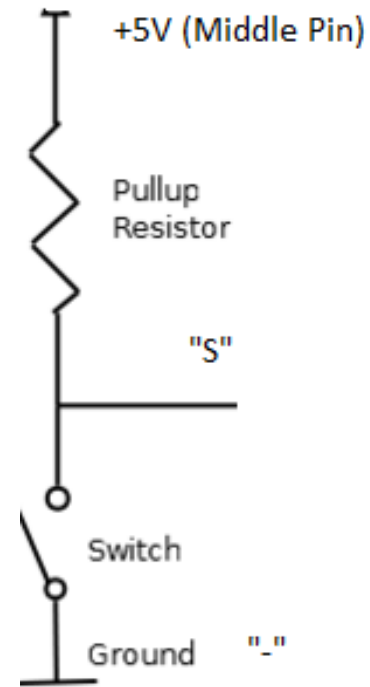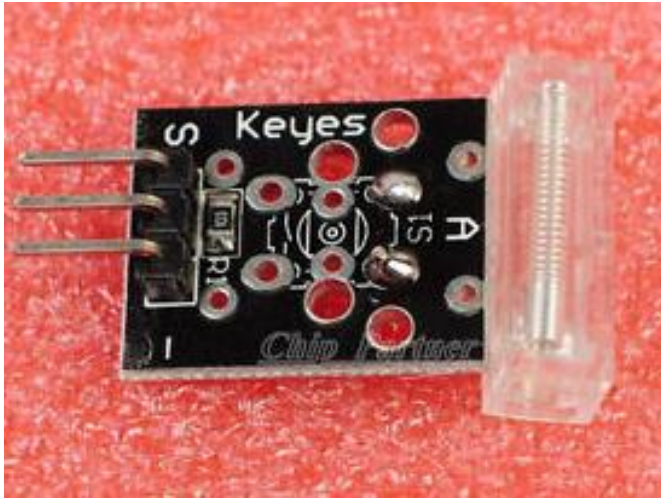



Pin "-" : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin "S" : Connect to Arduino Digital pin
configured to INPUT

Between Pin "S" and Middle Pin ("+5V")
there is 10 k Pull-up resistor


The code is as with
"simple button/key switch

Discuss usage in the industry and at home.

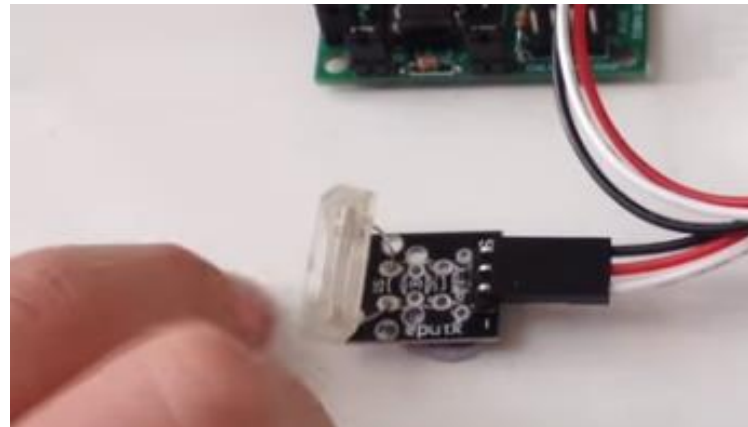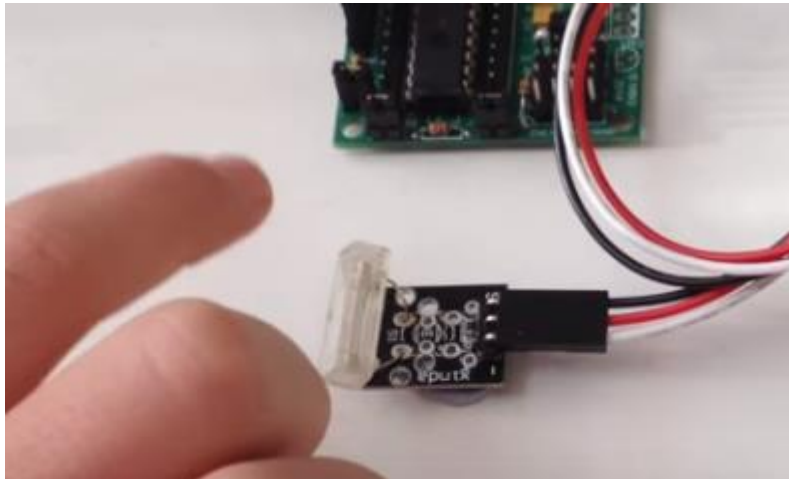**Operation of this module cannot be
demonstrated by using multimeter
(too slow)**





KY-017 Mercury tilt switch

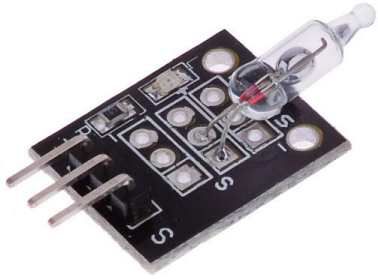

Pin “-” : Connect to Arduino GND
Middle pin : Connect to Arduino +5V
Pin “S” : Sensor Out

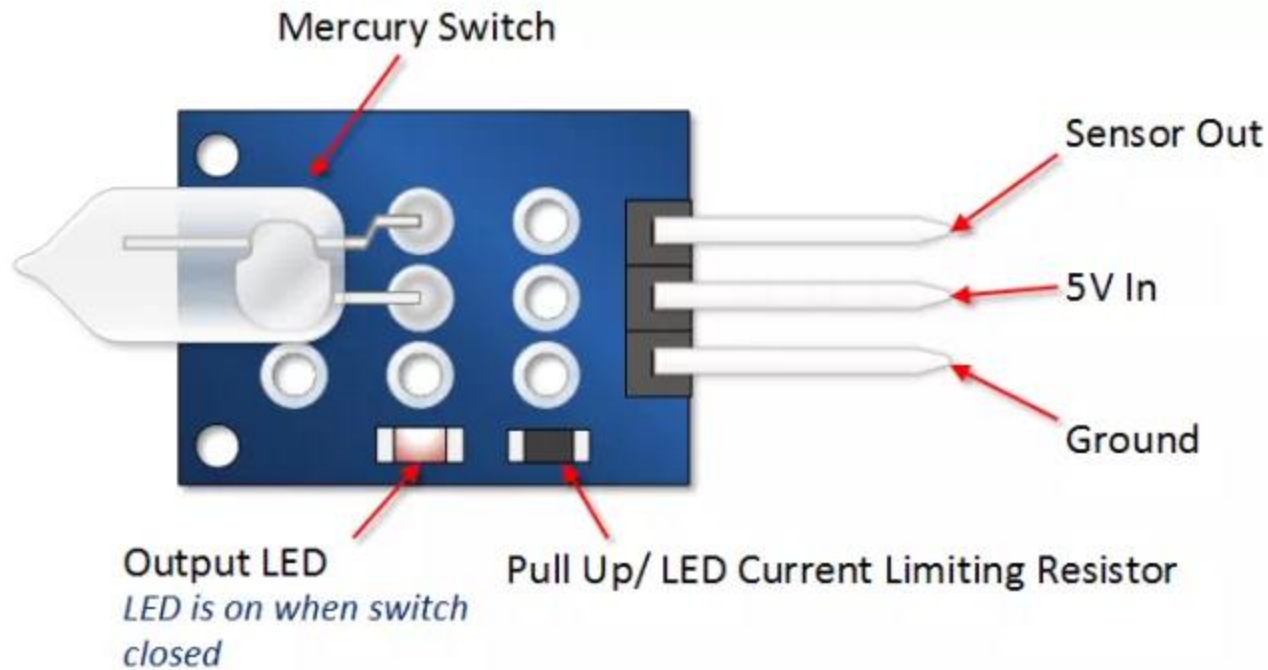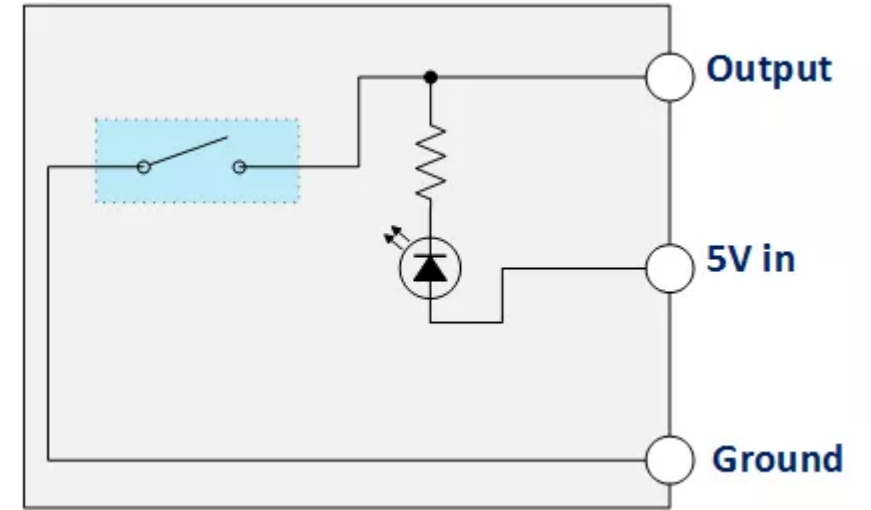Additionally
there is 10 k Pull-up resistor and LED



KY-017 Mercury tilt switch


Not Tilted

The code is as with
"simple button/key switch"

Tilted


The ball of mercury is shorting the switch contacts.

The output is LOW

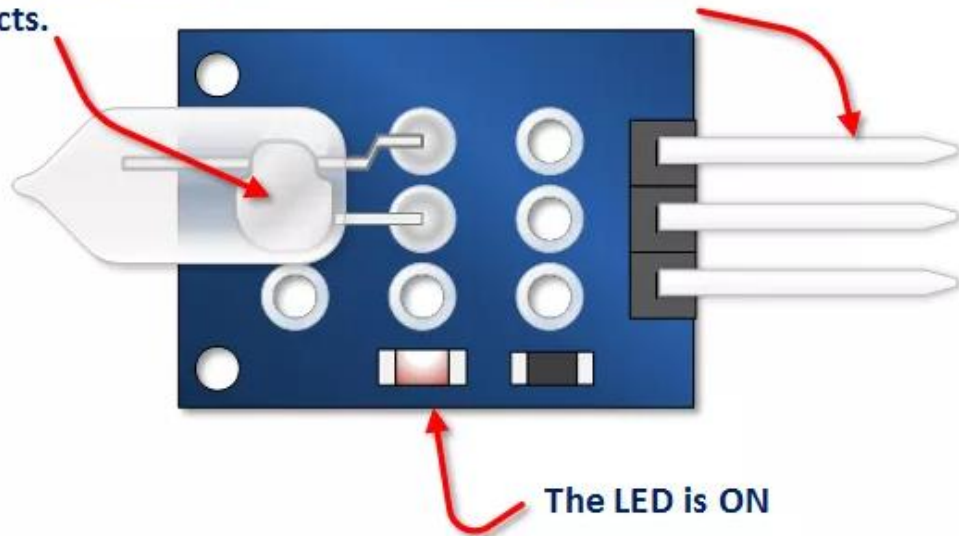

The ball of mercury is NOT shorting the switch contacts.

The output is High

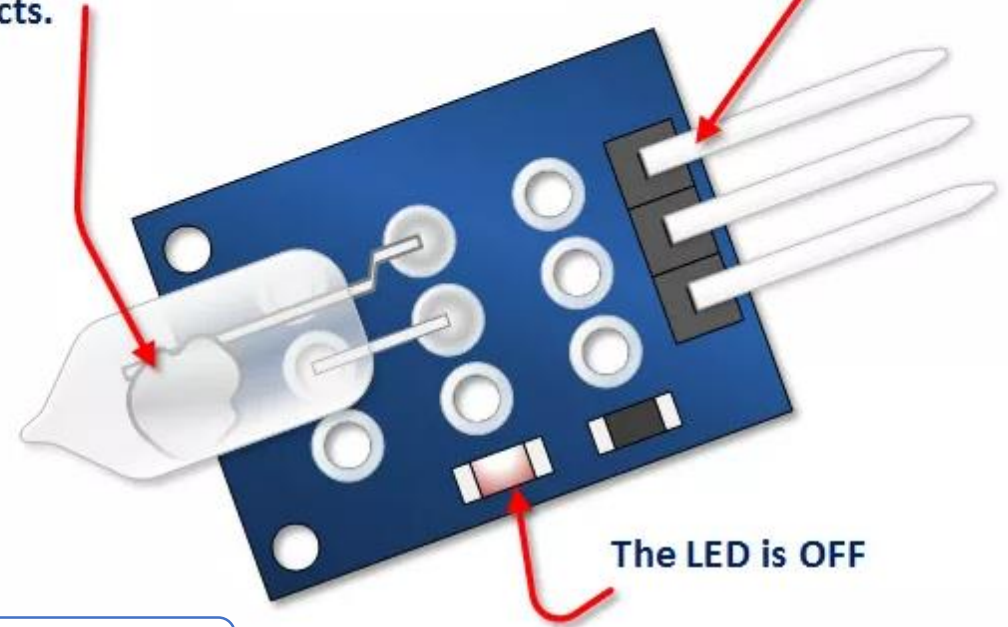

Discuss usage in the industry and at home.

Simple Actuators


37 Sensor Kit contains a number of simple ACTUATORS like LED, Buzzer.

In some cases operation of these modules can be demonstrated by applying +5V to relevant pins (do not forget about GND, however)

The simplest usage of these modules is to signal to human operator that something happen


LED as actuator.

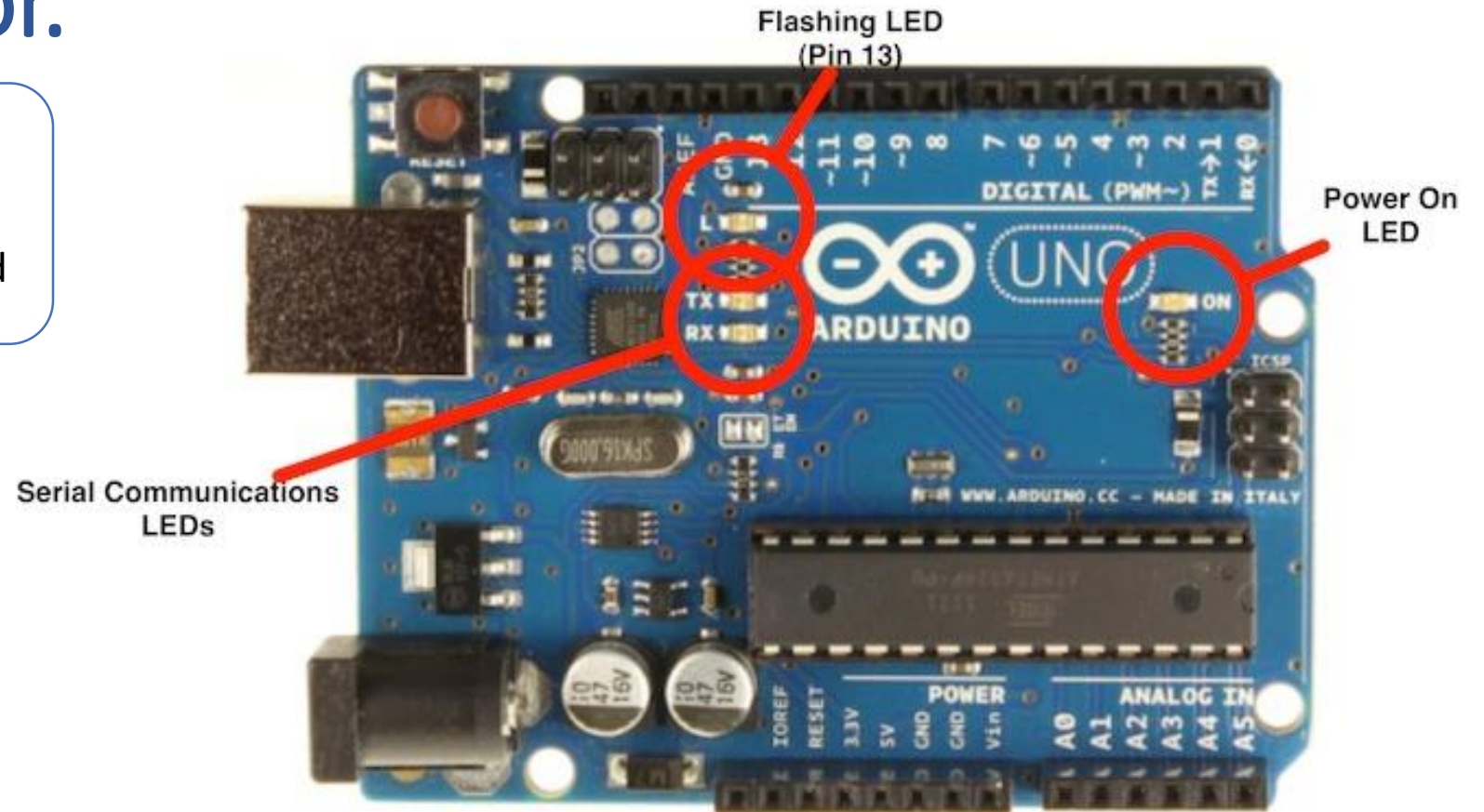We already know how to operate Flashing LED on the Pin13 of the Arduino Board



The trivial usage of the LEDs is to send to human operator simple predefined messages. For example “Power is ON”; Serial communication is going on

LED as actuator.

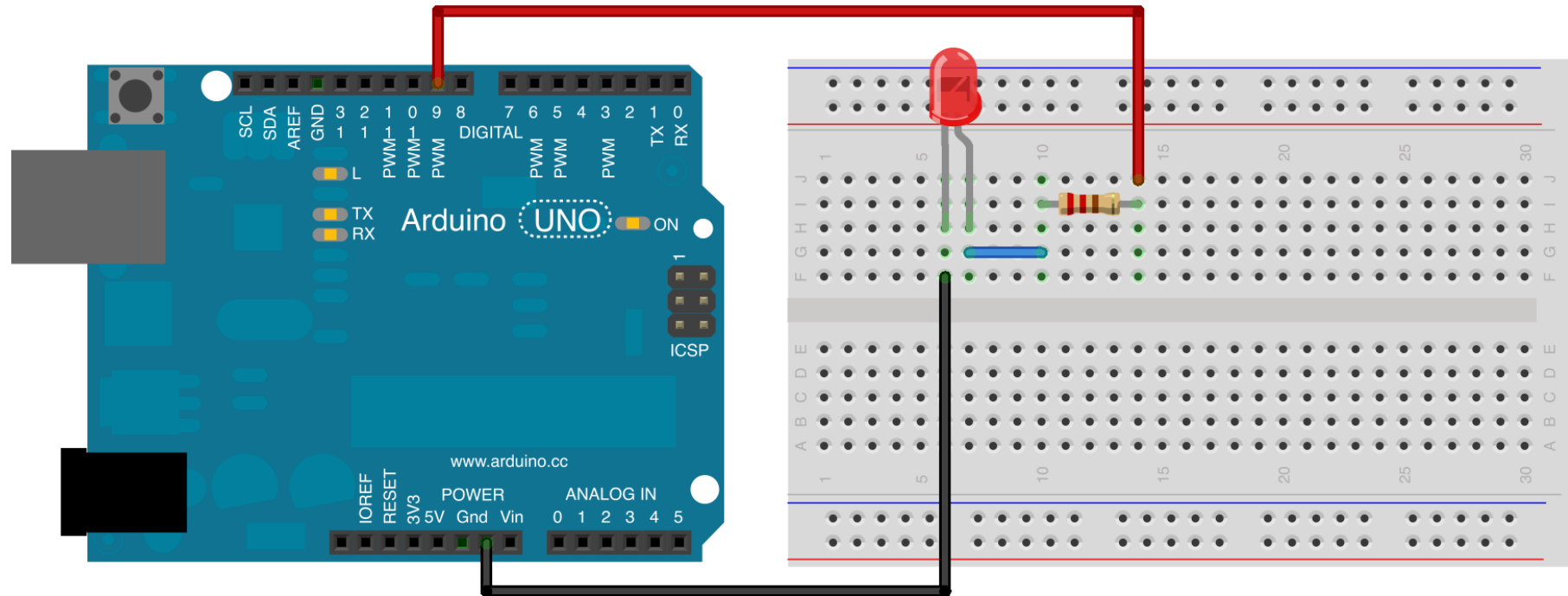

Made with  Fritzing.org

LED can be easily connected to Arduino.

BUT: As LED as Arduino board can be damaged in some cases.

→ Do not connect LEDs before checking voltages and currents.

Details later

KY-016 3-Color 5V RGB LED Module.

For some reason
known to producer only :

"R" == "B"

"G" == "G"

"B" == "R"



Demonstrate direct connection of R, G, B pins to 5V. Pin "-" to GND.
Safe, because protection resistors are on the module.

RGB trichromatic limiting resistor to prevent burnout

Advanced usage with PWM and analogWrite will be explained later

KY-009 3-Color 5V RGB SMD LED Module.


You can't connect the led's directly to the Arduino

→ You will need resistors!!

Arduino pin 9 > 180 Ohm resistor > Pin 'R' of KY009 module

Arduino pin 10 > 100 Ohm resistor > Pin 'G' of KY009 module

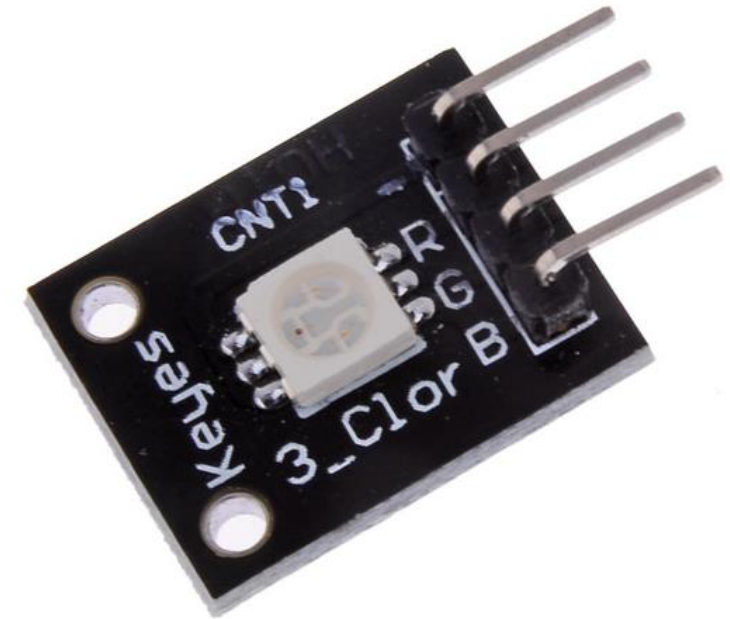
Arduino pin 11 > 100 Ohm resistor > Pin 'B' of KY009 module



No demonstrations

Students will not get this module (no reason)


KY-011 Two color LED 5mm .

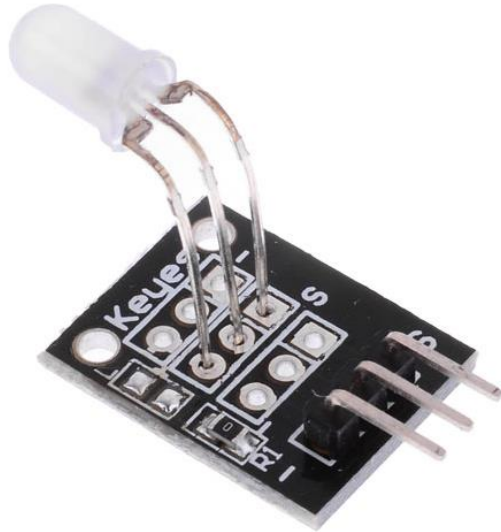

Color: Green + Red
Diameter: 5mm
Case Color: None
Package Type: Diffusion
Voltage (V) :2.0-2.5v
Using a current (MA): 10
Viewing angle: 150
Wavelength (NM): 571 +644
Luminous intensity (MCD) :20-40; 40-80
Stent type: long-legged
→ **330 Ohm resistor is needed**
→ **DO NOT USE**

No demonstrations
Students will not get this module (no reason)

KY-029 Two color LED mini 3mm diam.

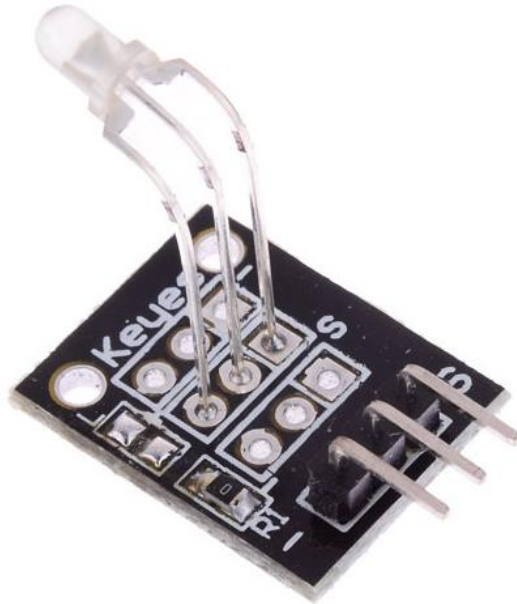

Color: Green + Red

Diameter: 3mm

Case Color: None

Package Type: Diffusion

Voltage (V) :2.0-2.5v

Using a current (MA): 10

Viewing angle: 150

Wavelength (NM): 571 +644

Luminous intensity (MCD) :20-40; 40-80


??? Ohm resistor is needed

→ DO NOT USE

No demonstrations

Students will not get this module (no reason)

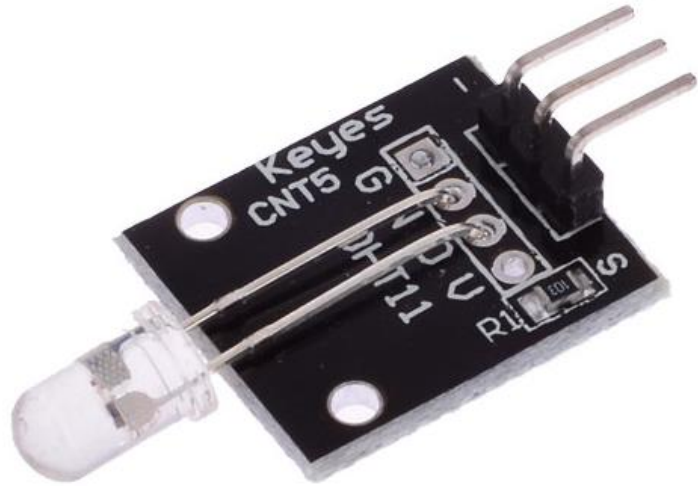KY-034 7-color Automatically Flashing LED



The module contains a 7-color 5mm LED with a built-in chip that sequentially flashes each color in turn. Color pattern is repeated in about **15 seconds**.

LED model: YB-3120B4PNYG-PM

Forward voltage: 2.5V - 6V

Forward current: 40mA

Connection

Pin	Description
"S"	+5V or +3.3V
Central	Ground
"_"	Not connected


Use as fancy ALARM.

Mind 15 sec time needed to see all the colors

Demonstrate by direct connection.

Attention: GND is Middle pin !!!

KY-008 Laser Diode 650 nm

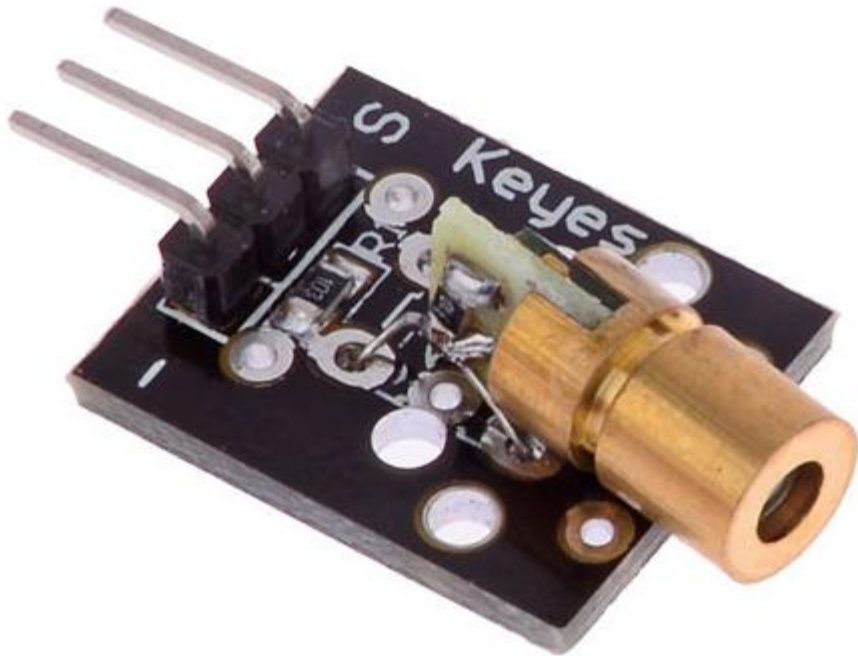


Connection

Pin	Description
"S"	+5V or +3.3V
Central	Not connected
"-"	Ground

Laser Diodes are widely used in electronics

BUT: Students will not get Laser Diode
Because this device is really dangerous.

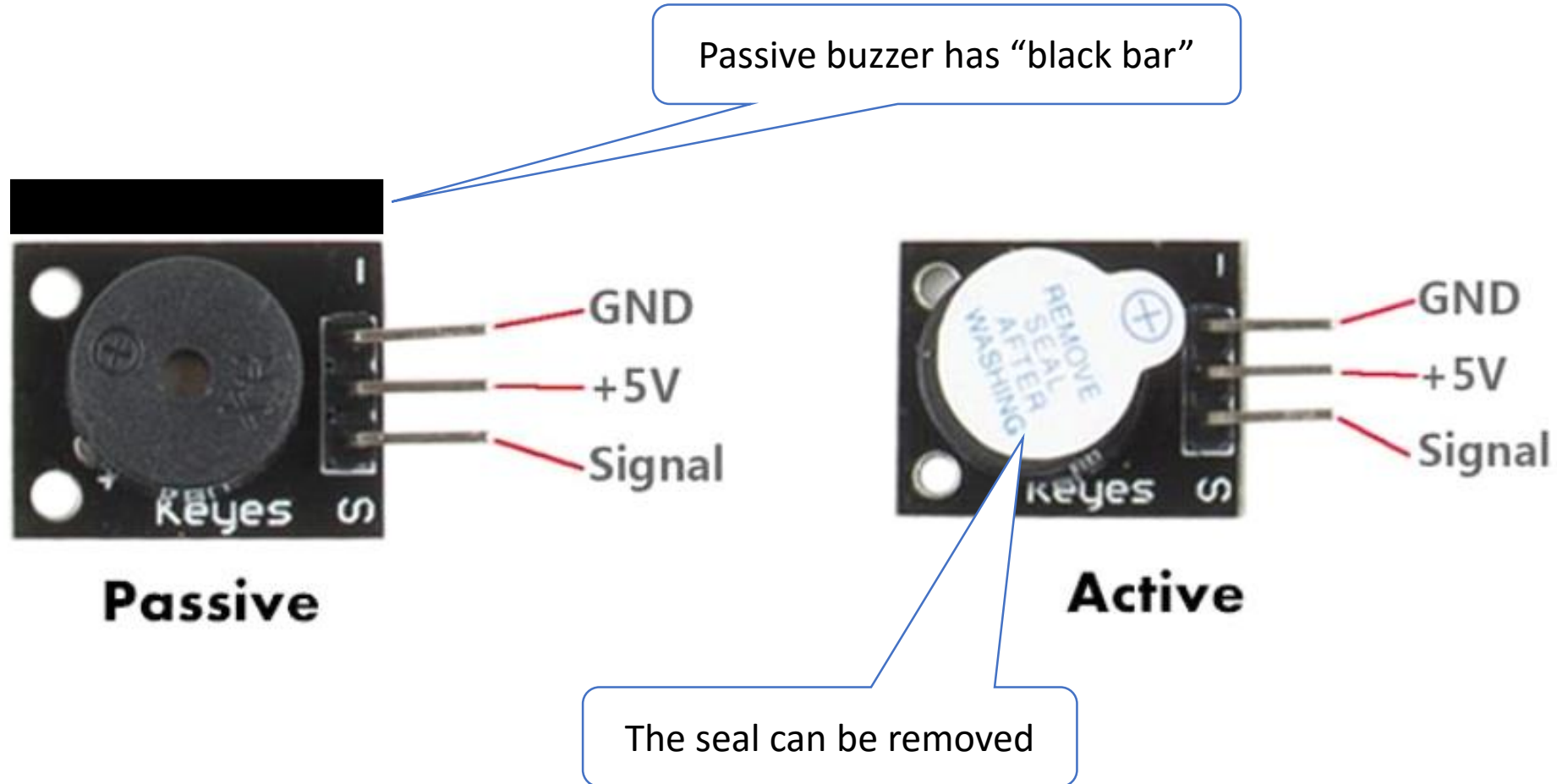KY-006 Passive Buzzer and KY-012 Active Buzzer



KY-006 Passive Buzzer and KY-012 Active Buzzer

Passive buzzer has passive piezo element inside



Active buzzer has piezo element and additional "oscillator" inside
→ More expensive, but simpler for usage



KY-006 Passive Buzzer and KY-012 Active Buzzer

Passive Buzzer

Can be used as Primitive Speaker
with limited frequency range)

Pin (-) : GND

Pin (S) : Signal

Middle pin is NOT USED

Connect "S" to pin producing "signal" of **different frequencies** → Buzzer will produce "sound"

Generally square wave (up to ~ 5K)
generated by digital pin is used.

When DC (5V) is connected to "S"
Only short "click" is heard.

Active Buzzer

Can be used as very simple **ALARM**

Pin (-) : GND

Pin (S) : Signal

Middle pin is NOT USED

When DC (or Pin having 5V or 3.3V)
is connected to "S" signal of
constant frequency is heard

KY-012 Active Buzzer

Active Buzzer

Can be used as very simple **ALARM together with LED13**

Pin (-) : Connect to GND

Pin (S) : Connect to (say) Pin 12

Middle pin is NOT USED

When Pin12 is low nothing happened

When Pin12 is HIGH "ALARM" is heard

**More sophisticated usage of active buzzer
with PWM will be discussed later**

KY-006 Passive Buzzer

Passive Buzzer can be used as a cheap alternative to speaker

BUT: Useful frequency range is limited

tone function

Syntax

tone(pin, frequency)

tone(pin, frequency, duration)

Parameters

pin: the pin on which to generate the tone

frequency: the frequency of the tone in Hertz - *unsigned int*

optional parameter: duration: the duration of the tone in milliseconds - *unsigned long*

Returns

nothing

For UNO:

min frequency: 31 Hz. Max frequency 65535 Hz

BUT:


**primitive buzzer cannot play such
a high frequencies.**

The alternative tone function can be implemented by direct manipulations with relative pin

KY-006 Passive Buzzer play melody


<https://www.arduino.cc/en/Tutorial/ToneMelody?from=Tutorial.Tone>

Circuit

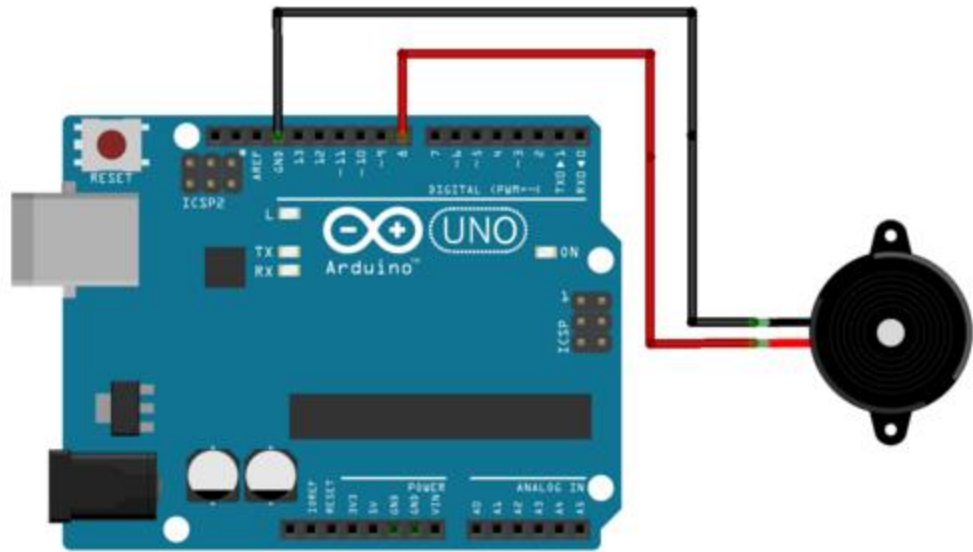

fritzing

Schematic

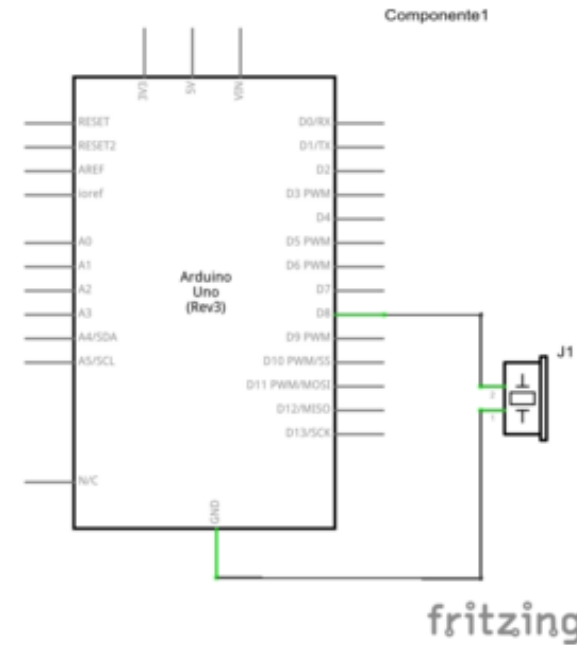

fritzing

Go to above page to see the code. **BUT: Use buzzer, not 8 Ohm speaker !!!!!**

Speaker instead of Passive Buzzer

If you connected the speaker directly to the Arduino digital pin you have damaged your Arduino pin by pulling too much current from it.

Do not rely on internal protection resistor.

You need at least a 120 ohm resistor in line with the speaker for direct connection. Of course it will not be as loud but then you are not burning your output pin.

For best results you need to use a transistor and capacitor to connect your speaker. Google for lots of schematics.


Translation: Use Power Amplifier with different Power Supply.

KY-019 5V Relay Module

<http://tinkbox.ph/sites/tinkbox.ph/files/downloads/KEYES%205V%20Relay%20Module%20KY-019.pdf>

Relay module with one normally open and one normally closed contacts.
It can be used to control home appliances up to **220V AC 10A or 30 V DC 10A.**

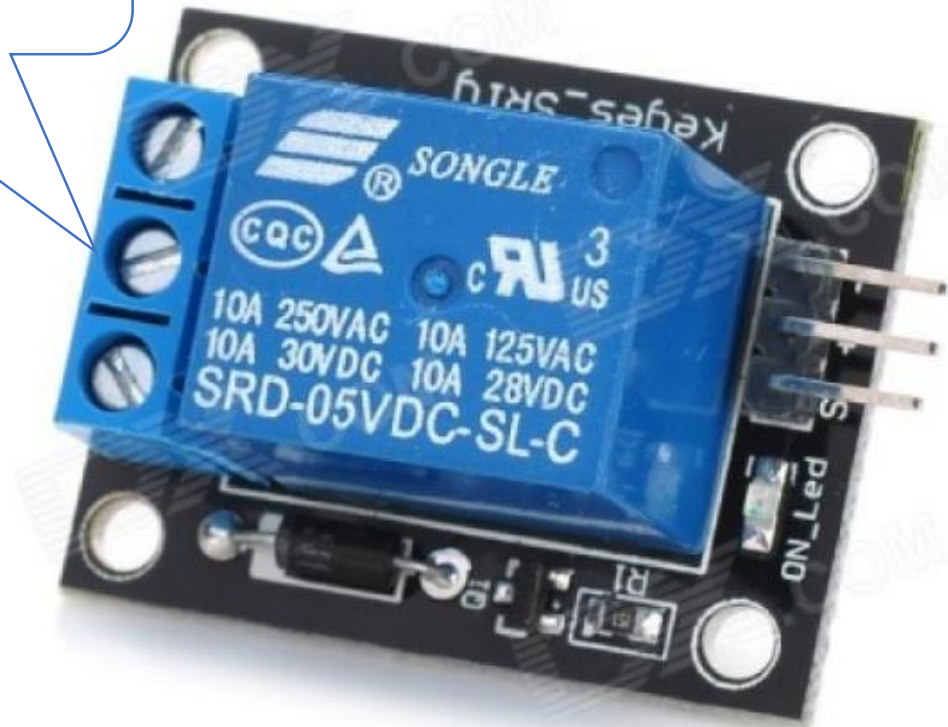Do not Connect serious staff here
REMEMBER: It case of 220 V
EE must think what and how can
be connected




“-” : GND
Middle Pin : “+5V”
“S” : Digital Signal

NC : Normally closed
NO : normally open
Common : common

KY-019 5V Relay Module

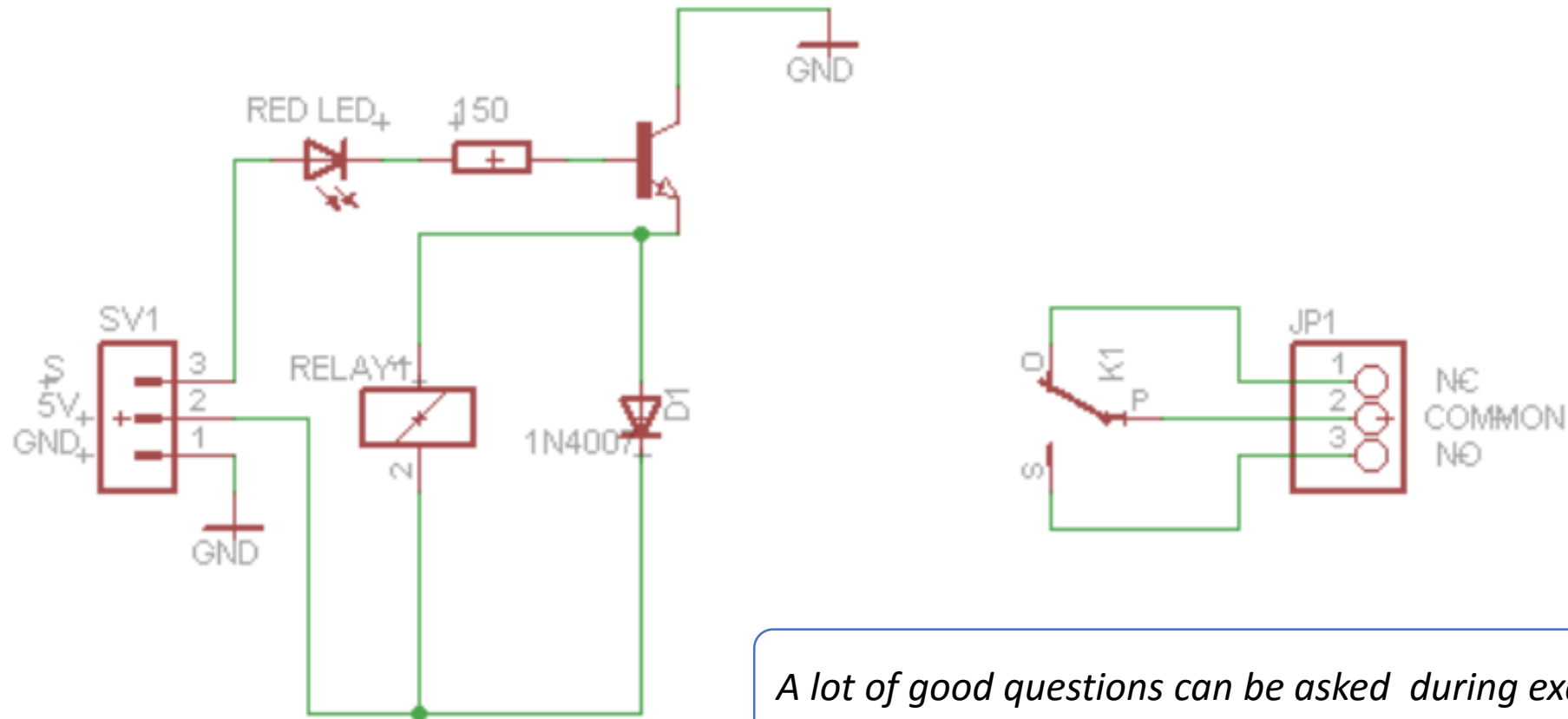
<http://tinkbox.ph/sites/tinkbox.ph/files/downloads/KEYES%205V%20Relay%20Module%20KY-019.pdf>



A lot of good questions can be asked during exam...

KY-019 5V Relay Module. Low Voltage connection

Wiring Diagram

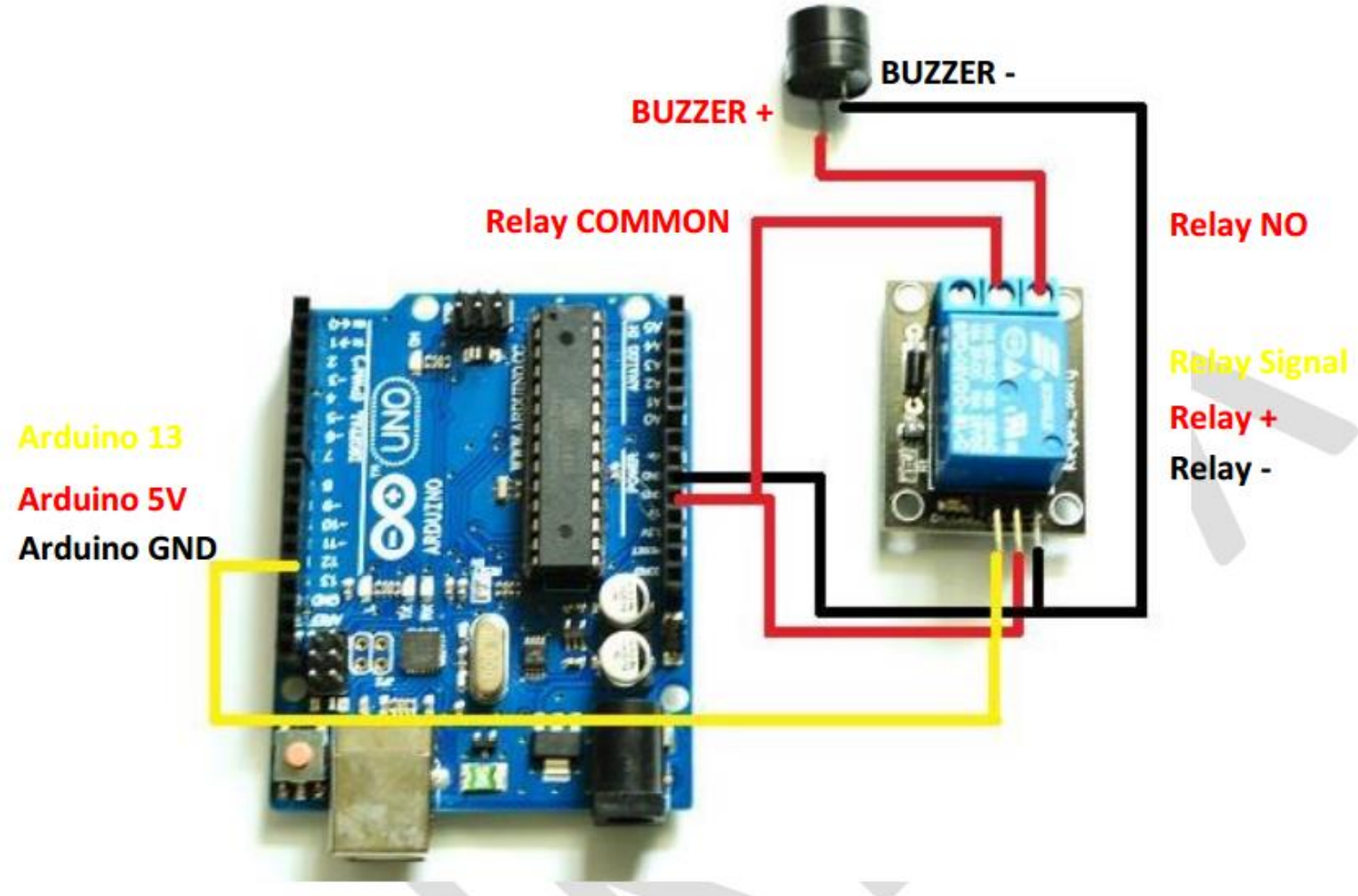

KY-019 5V Relay Module. Low Voltage connection

Sample Program

```
// Keyes 5V Relay Module Sample Program

void setup() {
  // initialize digital pin 13 as an output.
  pinMode(13, OUTPUT);
}

// the loop function runs over and over again forever
void loop() {
  digitalWrite(13, HIGH); // turn the 5V buzzer on
  delay(2000);           // on for two seconds
  digitalWrite(13, LOW); // turn the 5V buzzer off
  delay(2000);          // off for two seconds
}
```

The **buzzer** will turn on every two seconds. You can also hear the **tick of relay** every two seconds

Other Modules

Design and usage of other modules will be explained later.

Please do not use them before explanations